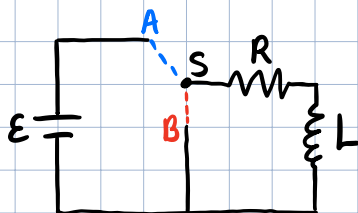


RL Circuit




Begin in position **A**:

$$\varepsilon - IR - L \frac{dI}{dt} = 0 \rightarrow dt = \frac{L dI}{\varepsilon - IR} \rightarrow t = -\frac{L}{R} \ln\left(1 - \frac{IR}{\varepsilon}\right) \rightarrow e^{-Rt/L} = 1 - \frac{IR}{\varepsilon} \rightarrow I = \frac{\varepsilon}{R} (1 - e^{-Rt/L})$$

$$V_L = -L \frac{dI}{dt} = -L \frac{d}{dt} \left[\frac{\varepsilon}{R} (1 - e^{-Rt/L}) \right] = -\varepsilon e^{-Rt/L}$$


$\tau = \frac{L}{R}$ is time constant

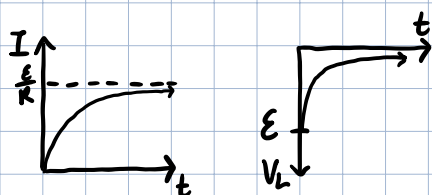

Switch to position **B**:

$$-IR - L \frac{dI}{dt} = 0 \rightarrow dt = -L \frac{dI}{IR} \rightarrow t = -\frac{L}{R} \ln\left(\frac{I}{I_0}\right) \rightarrow I = I_0 e^{-Rt/L} = \frac{\varepsilon}{R} e^{-Rt/L}$$
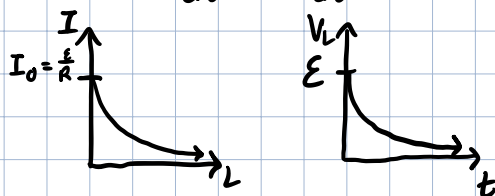
$$V_L = -L \frac{dI}{dt} = -L \frac{d}{dt} (I_0 e^{-Rt/L}) = \varepsilon e^{-Rt/L}$$




- We say that the energy of an inductor is stored in its magnetic field

$$\varepsilon - IR - L \frac{dI}{dt} = 0 \rightarrow \varepsilon I - I^2 R - L I \frac{dI}{dt} = 0 \rightarrow P = L I \frac{dI}{dt} = \frac{dU}{dt} \rightarrow L I dI = dU \rightarrow U = \frac{1}{2} L I^2$$

- Energy density: $u = \frac{U}{\text{vol}} = \frac{U}{\ell A} = \frac{L I^2}{2 \ell A} = \frac{\mu_0 \lambda^2 A I^2}{2 A} = \frac{B^2}{2 \mu_0}$

Mutual Inductance

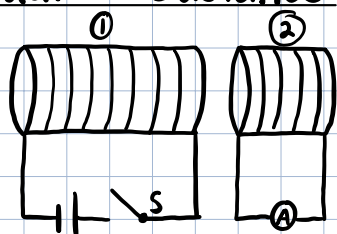

Close S: I_1 sets up $\frac{d\Phi_2}{dt}$

Mutual inductance of 2 with respect to I_1 : $M_{21} = \frac{N_2 \Phi_2}{I_1}$

Mutual inductance of 1 with respect to I_2 : $M_{12} = \frac{N_1 \Phi_1}{I_2}$

It can be shown that $M_{21} = M_{12} = M$ and $\varepsilon_1 = -M \frac{dI_2}{dt}$, $\varepsilon_2 = -M \frac{dI_1}{dt}$

Apparently if you have two inductors close enough, $\varepsilon_i = -L \frac{dI_i}{dt} - M \frac{dI_j}{dt}$