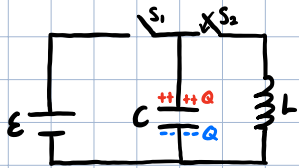


# LC Circuit



After  $S_1$  has been closed for a long time, open  $S_1$  and close  $S_2$ ; generates AC current


$$-\frac{q}{C} - L \frac{dI}{dt} = 0 \rightarrow \frac{q}{C} + L \frac{d^2q}{dt^2} = 0 \rightarrow \frac{d^2q}{dt^2} = -\frac{1}{LC} q \rightarrow q_c = Q \cos(\omega t), \omega = \sqrt{\frac{1}{LC}}$$

$$I = \frac{dq}{dt} = -Q\omega \sin(\omega t)$$

$$U_C = \frac{1}{2} \times \frac{q^2}{C} = \frac{Q^2}{2C} \cos^2(\omega t), U_L = \frac{1}{2} L I^2 = \frac{L Q^2 \omega^2}{2} \sin^2(\omega t) = \frac{Q^2}{2C} \sin^2(\omega t) \rightarrow U_{tot} = \frac{Q^2}{2C}; \text{energy conserved}$$

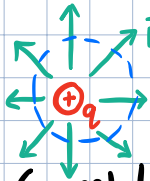
# Maxwell's Equations

- "Consolidated E + M equations"
- Gauss' Law for Electrostatics:



$$\Phi_E = \oint \vec{E} \cdot d\vec{A} = \frac{Q_{encl}}{\epsilon_0}$$

- Gauss' Law for Magnetism

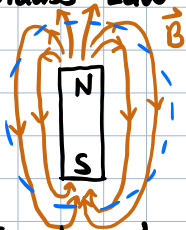


$$\Phi_M = \oint \vec{B} \cdot d\vec{A} = 0$$


- Faraday's Law of Induction

$$\mathcal{E} = \int \vec{E} \cdot d\vec{s} = -\frac{d}{dt} \int \vec{B} \cdot d\vec{A}$$

- Ampere - Maxwell Law

Ampere's Law:   $\oint \vec{B} \cdot d\vec{s} = \mu_0 I_{encl}$ ; doesn't work for everything

Charging a capacitor:

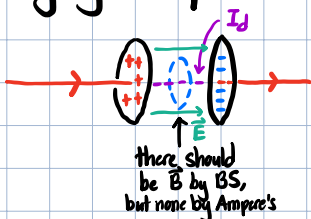

There's something "like a current"; displacement current  $I_d$

$$I_d = \frac{dq}{dt} = \frac{d}{dt}(C\mathcal{E}) = \frac{d}{dt}(\epsilon_0 \oint \vec{E} \cdot d\vec{A}) = \frac{d}{dt}(\epsilon_0 \oint \vec{E} \cdot d\vec{A})$$

$$\text{Ampere-Maxwell: } \oint \vec{B} \cdot d\vec{s} = \mu_0 [I_{encl} + I_d] = \mu_0 \left[ I_{encl} + \epsilon_0 \frac{d}{dt} \left( \oint \vec{E} \cdot d\vec{A} \right) \right]$$