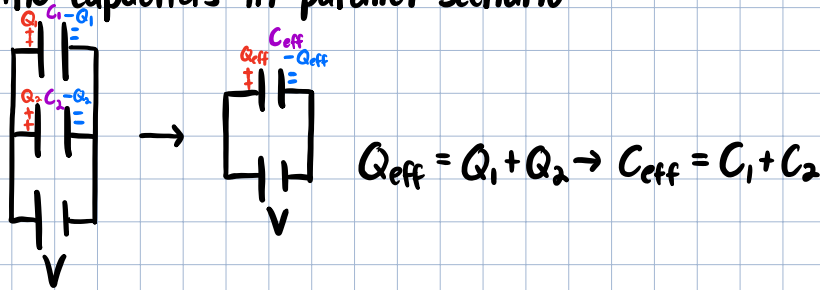


More Capacitors


- Recall the capacitors-in-parallel scenario



If $C_1 = 1\mu\text{F}$, $C_2 = 2\mu\text{F}$, and $V = 10\text{V}$, then:

$$C_{\text{eff}} = 3\mu\text{F}, Q_{\text{eff}} = C_{\text{eff}} \times V = 30\mu\text{C}, Q_1 = C_1 \times V = 10\mu\text{C}, Q_2 = C_2 \times V = 20\mu\text{C}$$


- What about capacitors in series?

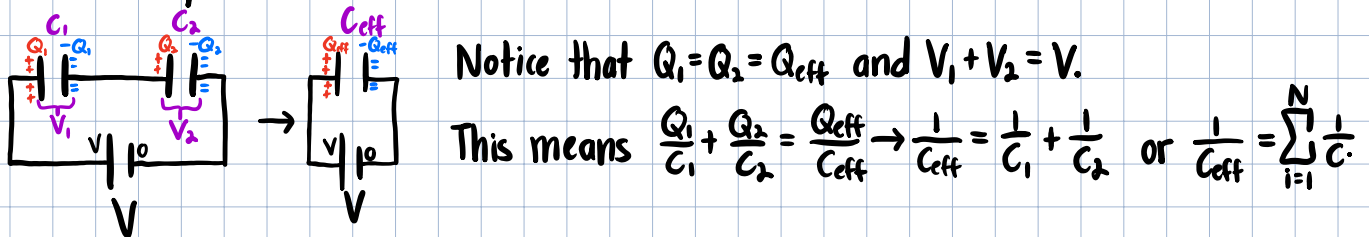

If $C_1 = 1\mu\text{F}$, $C_2 = 2\mu\text{F}$, and $V = 10\text{V}$, then:

$$C_{\text{eff}} = 0.67\mu\text{F}, Q_{\text{eff}} = C_{\text{eff}} \times V = 6.7\mu\text{C}, Q_1 = 6.7\mu\text{C}, Q_2 = 6.7\mu\text{C}, V_1 = \frac{Q_1}{C_1} = 6.7\text{V}, V_2 = \frac{Q_2}{C_2} = 3.4\text{V}$$


- Combo circuit:

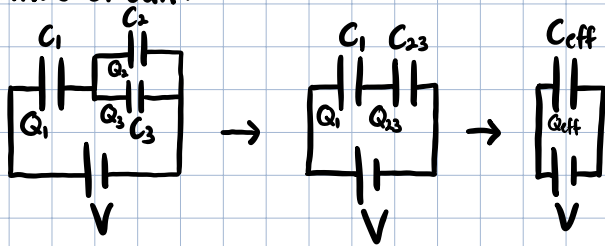

If $C_1 = 1\mu\text{F}$, $C_2 = 2\mu\text{F}$, $C_3 = 3\mu\text{F}$, and $V = 10\text{V}$, then:

$$C_{\text{eff}} = 0.83\mu\text{F}, Q_{\text{eff}} = C_{\text{eff}} \times V = 8.3\mu\text{C}, Q_1 = Q_{\text{eff}} = 8.3\mu\text{C}, V_1 = \frac{Q_1}{C_1} = 8.3\text{V}, C_{23} = 5\mu\text{F}, Q_{23} = Q_{\text{eff}} = 8.3\mu\text{C}, V_2 = \frac{Q_{23}}{C_{23}} = 1.66\text{V}, V_3 = 1.66\text{V}, Q_2 = 3.32\mu\text{C}, Q_3 = 4.98\mu\text{C}$$

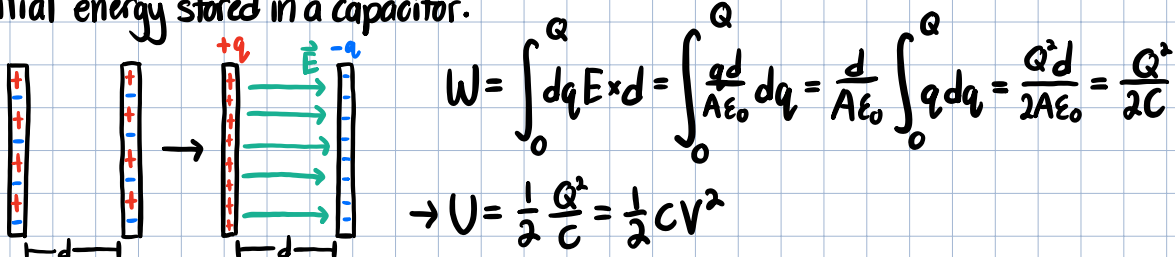- Potential energy stored in a capacitor:



• Energy density:

$$u = \frac{\text{energy}}{\text{volume}} = \frac{\frac{1}{2} \frac{dq^2}{A \epsilon_0}}{Ad} = \frac{1}{2} \times \frac{Q^2}{A \epsilon_0 d} = \frac{1}{2} \epsilon_0 E^2, \text{ "energy density"} \rightarrow U = \left(\frac{1}{2} \epsilon_0 E^2 \right) (Ad)$$