
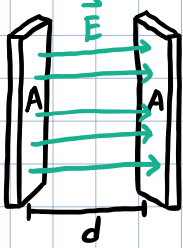

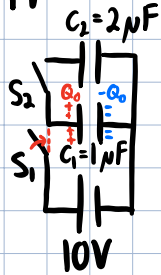
# Dielectrics

- Recall that for a capacitor, its energy is  $U = \frac{1}{2} Q^2 \frac{d}{A\epsilon_0} = \frac{1}{2} \times \frac{Q^2}{C} = \frac{1}{2} CV^2 = \underbrace{\overset{\text{energy density}}{\frac{1}{2} E^2 \epsilon_0}}_{\downarrow} A d$




- Suppose we have the following scenario:



If we close  $S_1$ , "for a long time",  $Q_0 = C_1 V = 10 \mu C$ .

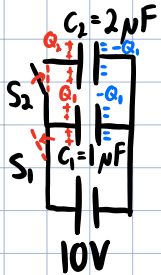$U$  stored in  $C_1 = \frac{1}{2} C_1 V^2 = 50 \mu J$



If we open  $S_1$  and close  $S_2$  "for a long time",  $V_{C_1} = V_{C_2} \rightarrow \frac{Q_1}{C_1} = \frac{Q_2}{C_2} \rightarrow 2Q_1 = Q_2$ .

We also know  $Q_0 = Q_1 + Q_2 \rightarrow Q_1 = 3.33 \mu C$  and  $Q_2 = 6.67 \mu C$ .

$U_1 = \frac{1}{2} \times \frac{Q_1^2}{C_1} = 5.56 \mu J$ ,  $U_2 = 11.12 \mu J \rightarrow U = 16.68 \mu J$


□ Why does  $U$  decrease?

- Energy is used to move the charges
- Charges are not as concentrated

- If we want square capacitors 1mm apart with capacitance  $1 \mu F$ , what should the side length be?

$$C = \frac{\epsilon_0 A}{d} = 10^{-6} = \frac{(8.85 \times 10^{-12}) \times x^2}{10^{-3}} \rightarrow x = 10.6 \text{ m}$$

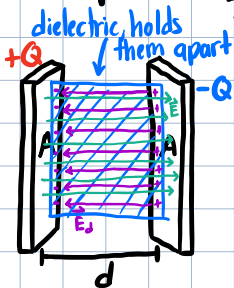- If we put an insulating material in a capacitor, it changes things referred to as dielectric



Without dielectric,  $C_0 = \frac{\epsilon_0 A}{d} = \frac{Q}{V_0} = \frac{Q}{E_0 d}$ .

With dielectric, atoms become slightly polarized, forming electric field  $E_d$  that goes against  $E_0$ .

$$C = \frac{Q}{V} = \frac{Q}{(E_0 - E_d)d} = KC_0 ; C > C_0, \frac{C}{C_0} = K = \text{dielectric constant.}$$


Note that  $E_0 = KE \rightarrow V = \frac{V_0}{K}$ .

- We can use Gauss' Law to find the electric field in a dielectric:

$$\oint \vec{E}_{\text{plates}} \cdot d\vec{A} = \frac{Q_{\text{plates}}}{\epsilon_0}$$

$$\rightarrow \oint K\vec{E} \cdot d\vec{A} = \frac{Q_{\text{plates}}}{\epsilon_0} \quad (\text{Idk check textbook})$$

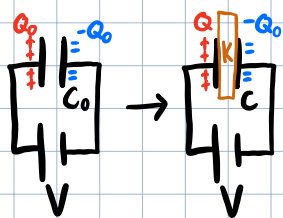- What if we put a dielectric in a circuit capacitor?



$$C = KC_0 \rightarrow \frac{Q}{V} = K \frac{Q_0}{V_0}; \quad V \text{ stays constant (battery)} \rightarrow Q = KQ_0.$$