
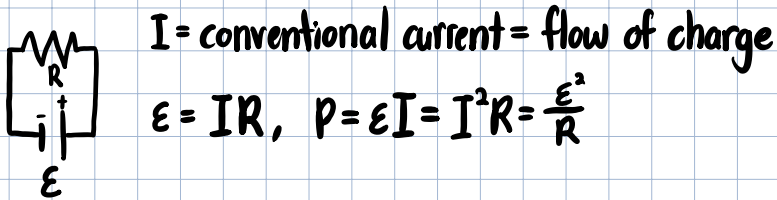


Direct Current Circuits

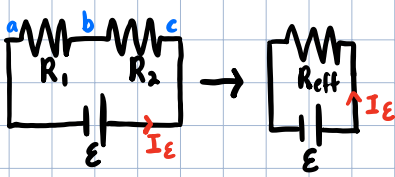- \mathcal{E} is called the "electromotive force" or "emf", but it's actually the voltage between two materials that make up the two terminals of a battery
- Simple circuit:



- Series circuit:




$$I_\mathcal{E} = I_{ab} = I_{bc} = I \quad \mathcal{E} = V_{ab} + V_{bc}$$

$$\rightarrow I_\mathcal{E} R_{\text{eff}} = I_{ab} R_{ab} + I_{bc} R_{bc} \rightarrow R_{\text{eff}} = R_{ab} + R_{bc}$$

So $R_{\text{eff}} = \sum_{i=1}^N R_i$.

- Parallel circuit:

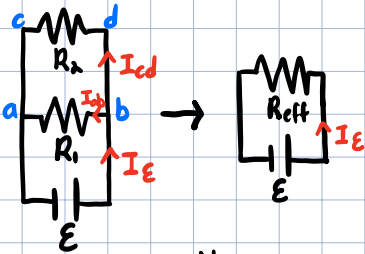


$$I_\mathcal{E} = I_{ab} + I_{cd} \quad \mathcal{E} = V_{ab} = V_{cd}$$

$$\rightarrow \frac{\mathcal{E}}{R_{\text{eff}}} = \frac{V_{ab}}{R_{ab}} + \frac{V_{cd}}{R_{cd}} \rightarrow \frac{1}{R_{\text{eff}}} = \frac{1}{R_{ab}} + \frac{1}{R_{cd}}$$

So $\frac{1}{R_{\text{eff}}} = \sum_{i=1}^N \frac{1}{R_i}$.

- In series, larger resistor dissipates more power whereas the smaller one does when in parallel

- Example:

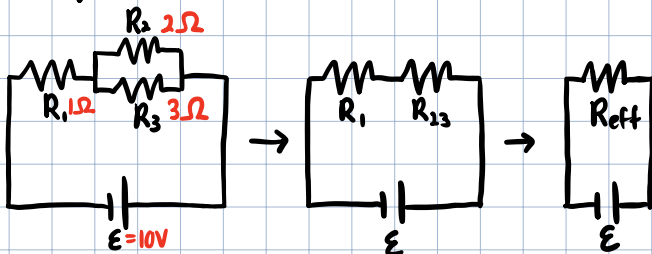

$$R_{\text{eff}} = 1 + \frac{1}{\frac{1}{2} + \frac{1}{3}} = 2.2\Omega \quad I_\mathcal{E} = \frac{10}{2.2} = 4.55A \quad P_\mathcal{E} = 10 \times 4.55 = 45.5W$$

$$I_1 = 4.55A \quad V_1 = 4.55 \times 1 = 4.55V \quad V_2 = 5.45V \quad V_3 = 5.45V$$

$$I_2 = \frac{5.45}{2} = 2.73A \quad I_3 = \frac{5.45}{3} = 1.82A \quad P_1 = 4.55^2 = 20.70W \quad P_2 = 14.88W \quad P_3 = 45.5W$$